

A

### Practice Problems

- Determine the total resistance, total current, and the currents through each branch of the following circuit.

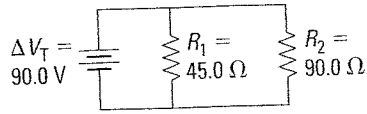


Figure 11.29

- Determine the total resistance, total current, and the currents through each branch of the following circuit.

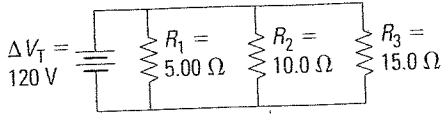


Figure 11.30

#### Answers

- $R_T = 30.0 \Omega$ ,  $I_T = 3.00 \text{ A}$   
 $I_1 = 2.00 \text{ A}$ ,  $I_2 = 1.00 \text{ A}$
- $R_T = 2.73 \Omega$ ,  $I_T = 44.0 \text{ A}$ ,  $I_1 = 24.0 \text{ A}$   
 $I_2 = 12.0 \text{ A}$ ,  $I_3 = 8.00 \text{ A}$

B

### Practice Problems

- Determine the current and potential difference through each resistor in Figure 11.38.

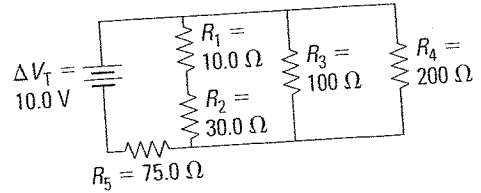


Figure 11.38

- Determine the current and potential difference through each resistor in Figure 11.39.

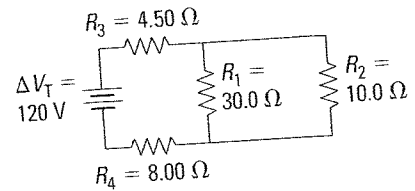


Figure 11.39


#### Answers

- $I_1 = 0.0625 \text{ A}$ ,  $I_2 = 0.0625 \text{ A}$ ,  
 $I_3 = 0.0250 \text{ A}$ ,  $I_4 = 0.0125 \text{ A}$ ,  $I_5 = 0.100 \text{ A}$ ,  
 $\Delta V_1 = 0.625 \text{ V}$ ,  $\Delta V_2 = 1.88 \text{ V}$ ,  $\Delta V_3 = 2.50 \text{ V}$ ,  
 $\Delta V_4 = 2.50 \text{ V}$ , and  $\Delta V_5 = 7.50 \text{ V}$
- $I_1 = 1.50 \text{ A}$ ,  $I_2 = 4.50 \text{ A}$ ,  $I_3 = 6.00 \text{ A}$ ,  $I_4 = 6.00 \text{ A}$ ,  
 $\Delta V_1 = 45.0 \text{ V}$ ,  $\Delta V_2 = 45.0 \text{ V}$ ,  $\Delta V_3 = 27.0 \text{ V}$ ,  
and  $\Delta V_4 = 48.0 \text{ V}$

Table 11.5 outlines the steps you can use to analyze mixed circuits when the resistances are known.

Table 11.5 Simplifying a Mixed Circuit

| Step   | Procedure   |
|--------|---|
| Step 1 | Reduce the circuit to a simple series circuit by using equivalent resistors.  |
| Step 2 | Determine the total resistance and total current of the series circuit using the equation for $R_T$ for series circuits and Ohm's law.                  |
| Step 3 | Determine the voltage drop across each resistor in the circuit using Ohm's law.   |
| Step 4 | Redraw the original circuit with the voltage drops beside each resistor. Remember that the voltage drop across the parallel resistors will be the same. |
| Step 5 | Determine the current through the parallel resistors using Ohm's law.   |

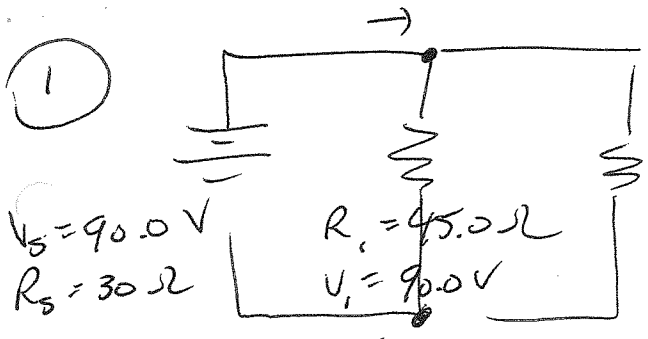

①  
 $V_s = 90.0\text{V}$   
 $R_s = 30\Omega$

$R_2 = 90.0\Omega$   
 $V_2 = 90.0\text{V}$

(A)

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$= \frac{1}{45} + \frac{1}{90}$$

$$= \frac{3}{90}$$

$$\frac{1}{R_{eq}} = \frac{3}{90}$$

$$\therefore R_{eq} = \frac{90}{3} = 30\Omega$$

$V_s = 90.0\text{V} \therefore V_1 = 90.0\text{V}$   
 $V_2 = 90.0\text{V}$   
KVL


$$I = \frac{V}{R}$$

$$\therefore I_s = \frac{90}{30} = 3.00\text{A}$$

$$I_1 = \frac{90}{45} = 2.00\text{A}$$

$$I_2 = \frac{90}{90} = 1.00\text{A}$$

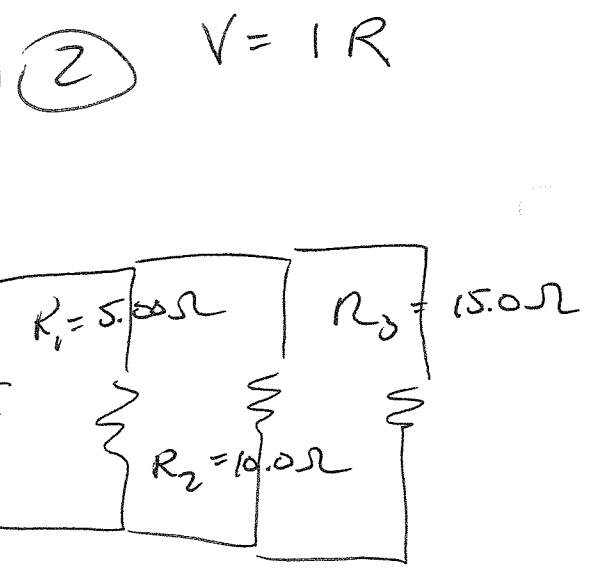current into junction = current out (3.00A)



\* Label circuit or create chart as you go

| source | 1     | 2    | 3    |      |
|--------|-------|------|------|------|
| R      | 2.73  | 5.00 | 10.0 | 15.0 |
| V      | 120V  | 120V | 120  | 120  |
| I      | 44.0A | 24   | 12   | 8    |

$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{10} + \frac{1}{15}$$

$$= \frac{6}{30} + \frac{3}{30} + \frac{2}{30} = \frac{11}{30}$$

$$R_e = \frac{30}{11} = 2.73\Omega = R_s$$

$$\therefore I_s = \frac{V}{R} = \frac{120}{2.73} = 44.0\text{A}$$


$$I_1 = 120/5 = 24$$

$$I_2 = 120/10 = 12$$

$$I_3 = 120/15 = 8$$

$$V = IR$$

B

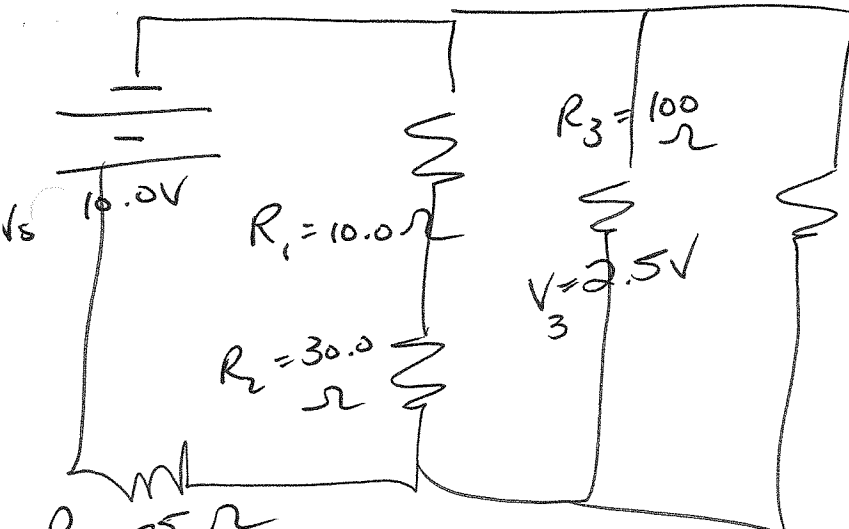

$R_5 = 75 \Omega$   
 $V_5 = 7.50 V$

|   | Source        | 1                  | 2                  | 3                  | 4                  | 5         |
|---|---------------|--------------------|--------------------|--------------------|--------------------|-----------|
| R | $18.2 \Omega$ | 10                 | 30                 | 100                | 200                | 75        |
| V | 10.0 V        | $0.625 V$          | $1.88 V$           | $2.5 V$            | $2.5 V$            | $7.50 V$  |
| I | $0.100 A$     | $\frac{0.0625}{A}$ | $\frac{0.0625}{A}$ | $\frac{0.0250}{A}$ | $\frac{0.0125}{A}$ | $0.100 A$ |

Find  $R_{eq} = R_5$       Multistep!

- 1<sup>st</sup> → Combine  $R_1/R_2$
- 2<sup>nd</sup> → Combine  $R_1/R_2$  with  $R_3, R_4$
- 3<sup>rd</sup> → Combine  $R_1/R_2/R_3/R_4$  with  $R_5$ !

$R_1$  with  $R_2$   
 $\frac{1}{\text{series}} \left\{ \begin{array}{l} \frac{1}{10.0 \Omega} \\ \frac{1}{30.0 \Omega} \end{array} \right\}$   
 $R_{eq} = 10.0 \Omega + 30.0 \Omega = \underline{\underline{40.0 \Omega}}$

$R_1/R_2$  with  $R_3 + R_4$   
 $\frac{1}{\text{parallel}} \left\{ \begin{array}{l} \frac{1}{40 \Omega} \\ \frac{1}{100 \Omega} \\ \frac{1}{200 \Omega} \end{array} \right\}$   
 $\frac{1}{R_{eq}} = \frac{1}{40} + \frac{1}{100} + \frac{1}{200}$   
 $= 0.025 + 0.01 + 0.005$   
 $= 0.04$   
 $\therefore R_e = \frac{1}{0.04} = 25 \Omega$

$R_1/R_2/R_3/R_4$  with  $R_5$        $R_{eq} = 25.0 + 75.0 = \underline{\underline{100 \Omega}}$

$$I_s = \frac{V_s}{R_s} = \frac{10.0}{100} = 0.100 \text{ A}$$

$R_s = R_{eq}$  of simplified circuit



$$\therefore I_s = 0.100 \text{ A} \quad \boxed{\text{KCL}}$$

$$V_s = IR$$


$$= (0.100)(75) = 7.5 \text{ V}$$

look @ 1 branch of circuit

$$V_s = V_3 + V_5 \quad \boxed{\text{KVL}}$$

$$10.0 = V_3 + 7.5$$

$$V_3 = 2.5 \text{ V}$$

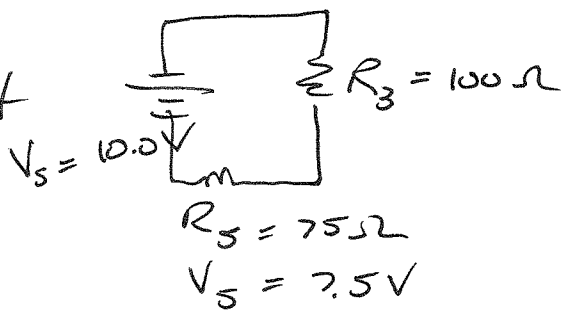


look @ another branch

$$\boxed{\text{KVL}} \quad V_s = V_4 + V_5$$

$$10.0 = V_4 + 7.5$$

$$V_4 = \underline{2.5 \text{ V}}$$

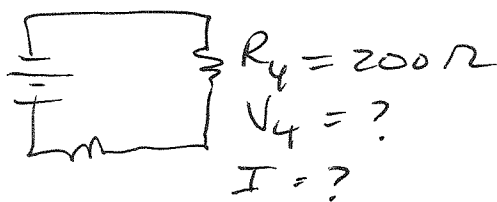

I don't know how 1 & 2 share voltage


Current

$$\#3 \quad I_3 = \frac{V_3}{R_3} = \frac{2.5 \text{ V}}{100} = 0.0250 \text{ A}$$

$$\#4 \quad I_4 = \frac{V_4}{R_4} = \frac{2.5}{200} = 0.0125 \text{ A}$$

OK... current & voltage thru 1 & 2

\* Look @ this branch.

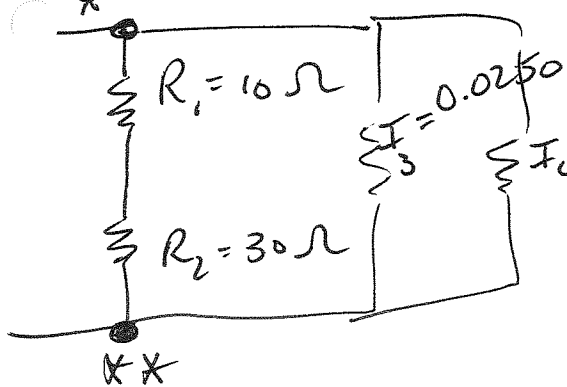

(KCL)  $\Rightarrow$  current going in to junction\*  
(0.100 A) = current going out  
of junction \*\*

$$I_5 = 0.100 \text{ A (going in)}$$

$$\therefore 0.100 = 0.0250 + 0.0125 + I_{1,2}$$

(#3)                    (#4)                    (thru #1 and #2)

$$\therefore I_{1,2} = 0.100 - 0.0375$$

- same bc in series

$$I_{1,2} = \underline{0.0625 \text{ A}}$$

---

OK  $V = IR$

$$V_1 = I_1 R_1 = (0.0625)(10) = 0.625 \text{ V}$$

$$V_2 = I_2 R_2 = (0.0625)(30) = 1.88 \text{ V}$$